




**MOTOROLA**  
Semiconductor Products Inc.

## **AN-864** Application Note

# **INTERFACING MULTIPLEXED BUS PERIPHERALS WITH NON-MULTIPLEXED MPUs**

 quantum electronics  
Box 391262  
Bramley  
2018

### **INTRODUCTION**

In general, 8-bit microprocessor buses may be divided into two major groups: multiplexed and non-multiplexed. A microprocessor (MPU) which has a non-multiplexed bus configuration requires two separate buses: an address bus and a data bus. However, an MPU which has a multiplexed bus configuration shares one bus for both address and data; i.e., the lower eight bits of address are output on the same lines that are used for the data bus. To accomplish this, a multiplexed bus cycle must be divided in two parts. During the first part of the cycle, the lower eight bits of address are output on the multiplexed bus pins. During the second part of the cycle, data is input or output via the multiplexed bus pins.

It is important that the two parts of the cycle be identified by both the multiplexed and non-multiplexed MPUs. For this reason, an address strobe line (AS or ALE) is used to indicate when the address is valid. During the second part of the cycle, the multiplexed bus lines are used to transfer data, and a data strobe line (DS) is used to indicate this.

Interfacing a multiplexed bus MPU (such as MC6803 or MC146805E2) with non-multiplexed bus peripherals is relatively straightforward. The interface can be accomplished by simply providing an external latch to capture the multiplexed address for the entire bus cycle. However, providing an interface between a non-multiplexed bus MPU (such as the MC6800 and the MC6809) and multiplexed bus peripherals is more difficult.

Generating the required address and data strobes, while also guaranteeing that the address and data are on and off the multiplexed bus at the required times, is not possible with

most non-multiplexed MPUs. Methods for providing an interface between non-multiplexed bus MPUs and multiplexed bus peripherals are discussed below.

### **SUGGESTED INTERFACING METHODS**

One method that is often used, but is not too efficient, employs the I/O lines of a peripheral interface adapter (PIA) to provide the multiplexed bus signals to the peripherals. This method, while fine for single-chip computers, requires excessive software, I/O lines, and execution time.

Another method, for allowing a non-multiplexed bus MPU to read or write multiplexed bus peripherals, is to consider the multiplexed bus as a two-register device. One register could be the address latch and the other could be the data register. By connecting the non-multiplexed bus to the multiplexed bus, as shown in Figure 1, the address strobe (AS) is generated by any MPU write to an even address (A0 is low). Although AS causes the state of the multiplexed pins to be captured in the address latch, no data is transferred until the data strobe (DS, RD, or WR) is generated. The data strobe is not generated until a specific decoded, odd address occurs; i.e., A0 is high. Thus, a valid access can only be made by first writing to the location (\$00-\$3F) of the byte to be accessed at an even address, and then by either reading from or writing to the decoded odd address. The software subroutine required to generate the address strobe (AS) and data strobe (DS) signals for the interface shown in Figure 1 is listed in Figure 2. The location to be accessed is contained in accumulator A and data is transferred via accumulator B. The following example clears register A (location \$0A) and then reads the data at location \$25.

### **SUPPLIED BY;**

P.O. Box 2944, Johannesburg 2000.  
Commerce Crescent  
Eastgate Ext 12  
Kramerville  
Sandton  
Tel: (011) 802-4107  
Telex: 4-27811



advanced semiconductor devices (Pty.) Ltd.

©MOTOROLA INC., 1982


and saved

quired for interfacing a competitor's non-multiplexed MPU

Both the MC146818 and MC146823 are CMOS devices

disables  $\overline{\text{CE}}$  and prevents any further MPU accesses.

## the MC

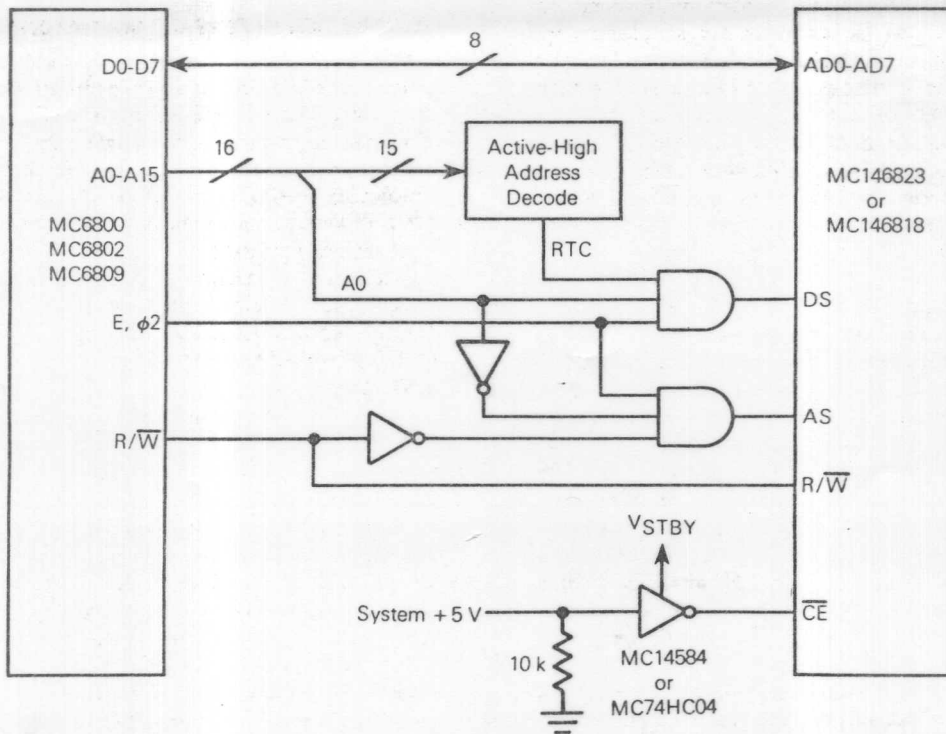

### Non-Multiplexed Bus Interface Schematic Diagram

READ	STAA	RTC	Generate AS and latch data from ACCA
	LDAB	RTC + 1	Generate DS and load ACCB with data read
	RTS		Return
WRITE	STAA	RTC	Generate AS and latch data from ACCA
	STAB	RTC + 1	Generate DS and store data from ACCB
	RTS		Return

FIGURE 2 — Subroutine for Controlling Interface  
Between Non-Multiplexed Bus and  
MC146818/MC146823

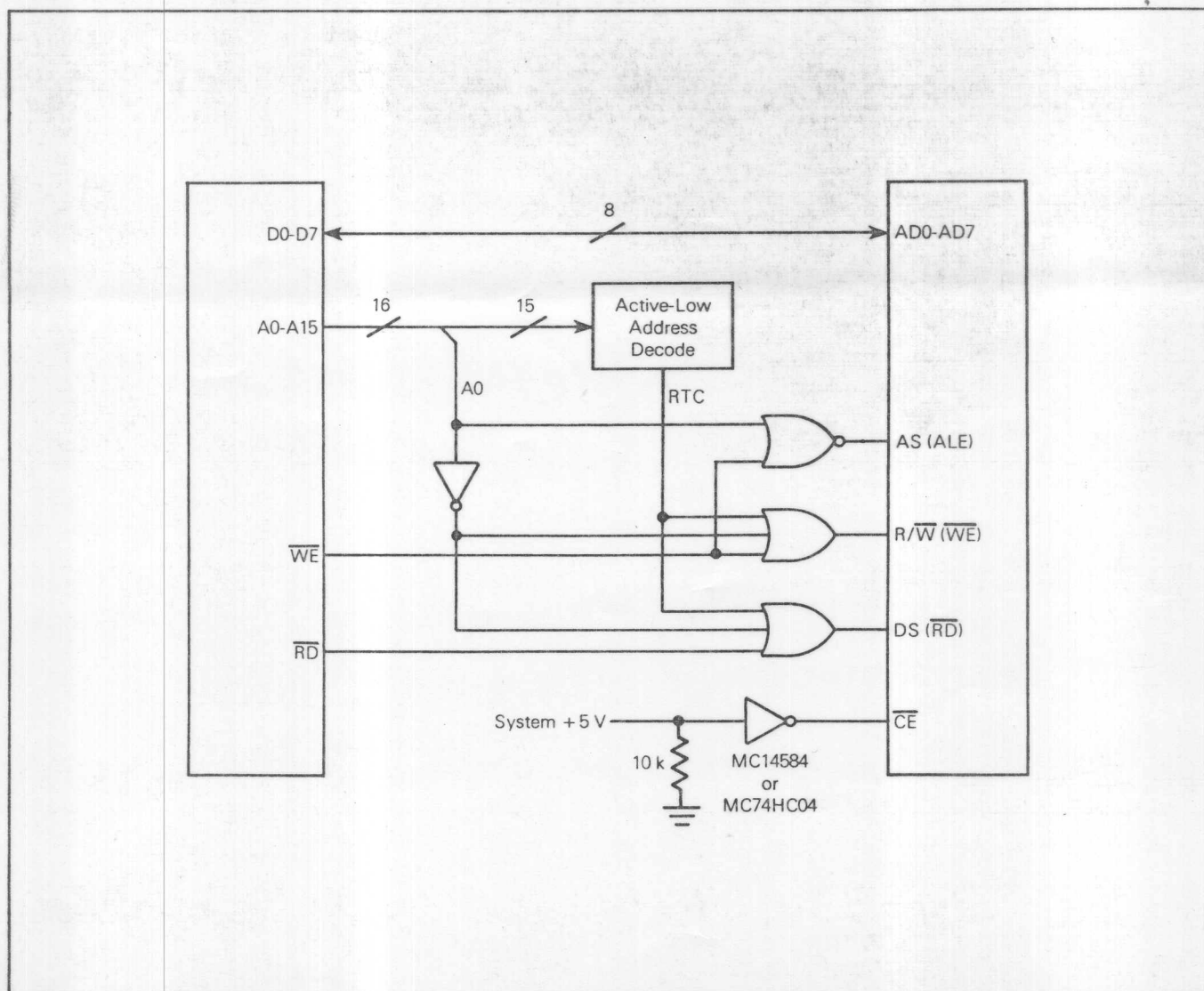


FIGURE 3 — MC146818/MC146823 and Competitor MPU  
Non-Multiplexed Bus Interface Schematic Diagram